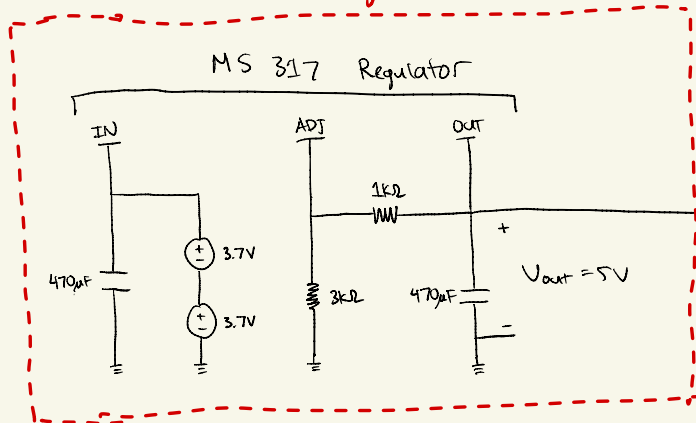



Bravo 6 - Main Circuit Diagram

7.4V → 5V Regulator circuit





5V

Camera circuit

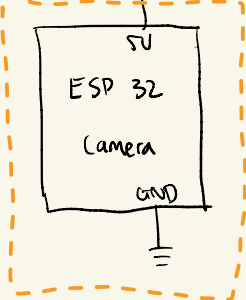


Servo motor circuit

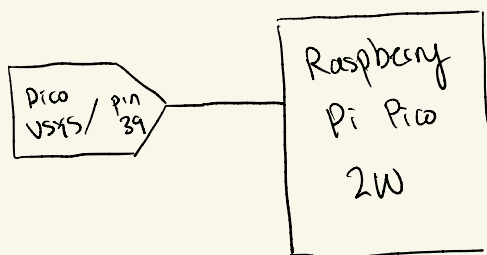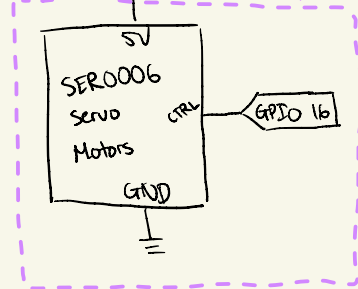


3.3V

photoresistor circuit

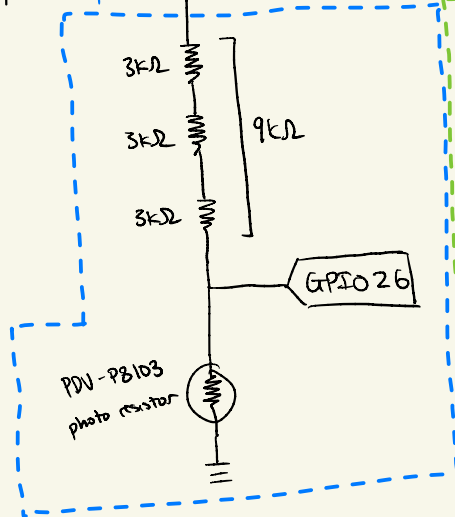


temperature & humidity circuit

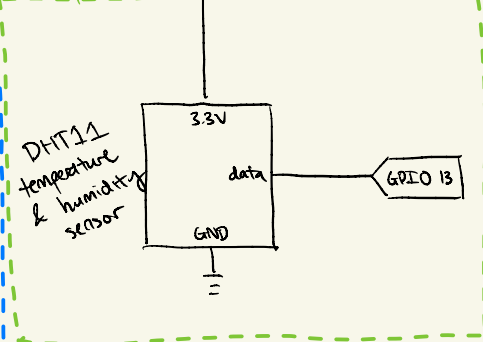

3.3V

ultrasonic sensor circuit

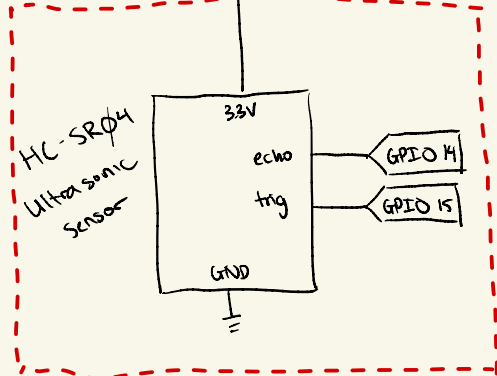

OLED display circuit

